

Registration No.:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 03

Course: B.Tech/IDD
Sub_Code: 23ES1001

1st Semester Regular/Back Examination: 2024-25

SUBJECT: BASIC ELECTRICAL ENGINEERING

BRANCH(S): AEIE, AUTO, BIOTECH, CHEM, CIVIL, CE, CST, CSEAI, CSEDS, CSE, CSEAIME, EEE, ELECTRICAL, ECE, ETC, MANUTECH, MECH, MME, METTA, MINERAL, PLASTIC

Time: 3 Hours

Max Marks: 100

Q.Code: R582

Answer Question No.1 (Part-I) which is compulsory, any eight from Part-II and any two from Part-III.

The figures in the right hand margin indicate marks.

Part-I

Q1 Answer the following questions: (2 x 10)

- The nodal analysis and mesh analysis of an electrical circuit is based on which laws?
- Explain how current source with a source resistance can be converted into an equivalent voltage source with simple example.
- State Super-position theorem.
- If two incandescent lamp of rating 100W, a fan rated 80W and a heater rated at 1000W are operated for 5 hr/day, calculate the total energy consumption in 7 days.
- A 250 V, 50 Hz supply is connected to a pure inductor. The resulting current is 1.5 A. Calculate the value of the inductance.
- The Magneto Motive Force of magnetic circuit is analogous to which quantity of electrical circuit? What is the reciprocal of permeability?
- What is the function of commutator in DC machines?
- What is the purpose of using core in a transformer and what are its features?
- What will happen if the slip of induction motor becomes zero?
- What are the different sources of electrical power?

Part-II

Q2 Only Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve) (6 x 8)

- What are the types of DC machine based on their excitation? Explain with circuit diagram.
- A 220 V shunt motor having armature resistance of 0.4 ohms takes an armature current of 30 A on a certain load. By how much must the main flux be reduced to raise the speed by 30% if the developed torque is constant? Neglect saturation and armature reaction.
- Explain the principle of operation of a single-phase transformer.
- Draw the vector diagram of a single-phase transformer for resistive, inductive, and capacitive loads considering winding resistances and magnetic leakage.
- Explain about layout of distribution system with neat sketch.

- f) Calculate the supply voltage V in the circuit shown in Figure 1.

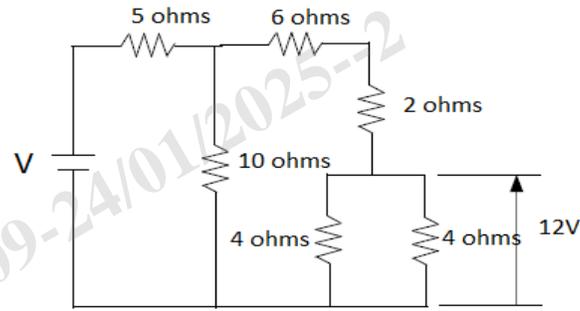


Fig. 1

- g) Determine the voltage v in the circuit shown in Figure 2. Use nodal analysis method.

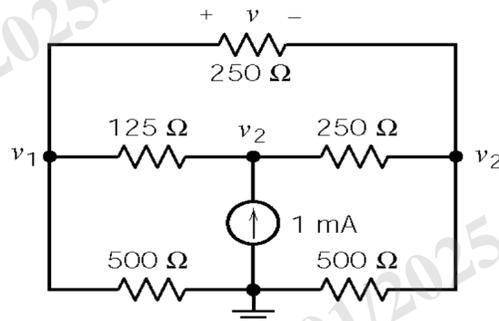


Fig. 2

- h) Draw Thevenin's equivalent circuit of the circuit shown in Figure 3.

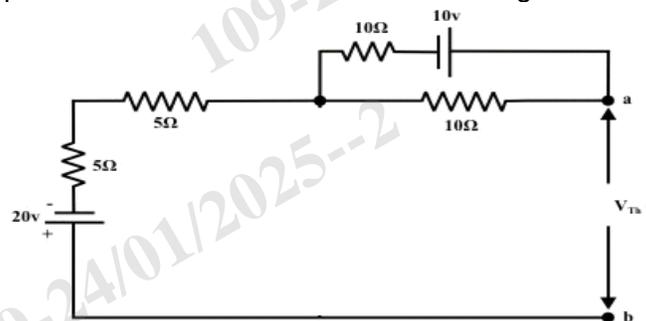


Fig. 3

- i) A total current of 1 A is drawn by the circuit shown in Figure 4 fed from an ac voltage, V of 50 Hz. Find the input voltage.

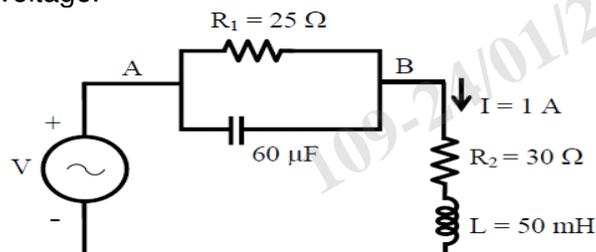


Fig. 4

- j) Explain the concept of resonance in series RLC circuit and derive the expression for resonance frequency. Also, plot the related curves.

- k) Three identical impedances connected in star fashion draw a line current of $(5\angle -30^\circ)$ A, when connected across a 400V, 50 Hz, three phase AC supply. Find the resistance, reactance, and impedance per phase.
- l) Explain the term “coefficient of coupling”. Two coils having self-inductances of 250 μ H and 150 μ H are magnetically coupled and connected in series opposition. Determine the effective inductance if the coefficient of coupling is 0.1.

Part-III

Only Long Answer Type Questions (Answer Any Two out of Four)

- Q3** Derive the formula for conversion of star connected resistances to delta connected resistances and vice-versa. Also, find the equivalent resistance R_{ab} in the circuit shown in Figure 5. (16)

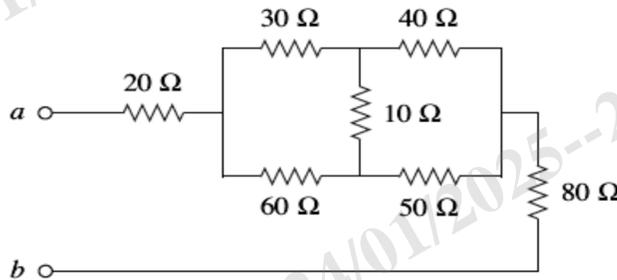


Fig. 5

- Q4** Define average value, RMS value, form factor and peak factor. Find the average value, RMS value, form factor and peak factor of the waveform shown in Figure 6. (16)

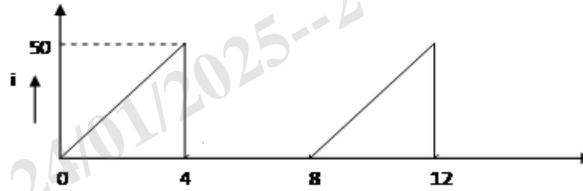


Fig. 6

- Q5** a) Explain the operating principle of a three phase induction motor and draw its torque-slip characteristic. (8x2)
- b) A 3-phase, 400 V, 50 Hz, 6 pole induction motor while rotating has frequency of rotor EMF 2 Hz. Calculate the slip, the rotor speed, and speed of stator field with respect to rotor.

- Q6** Draw the layout of electric power supply system. With neat diagram explain the layout of hydro-electric power plant. (16)